

1. Find a matrix whose square is σ_x .

Hint: There are lots of ways of doing this. One way is to first find a matrix whose square is σ_z .

2. **Making a SWAP gate**

Show how to create a SWAP gate using 3 CNOT gates.

3. **Controlled Hadamard gate**

Write down the 8×8 matrix that corresponds to a controlled Hadamard gate where the control is bit 3 and the target is bit 1.


4. **The Fredkin gate**

The Fredkin gate is a classical reversible three-bit gate. If the input is (x, y, z) , then the output is $(0, y, z)$ if $x = 0$ and $(1, z, y)$ if $x = 1$. In other words, it is a controlled SWAP: if x is 0, you do nothing, and if x is 1, you swap y and z .

- Show how you can obtain the gates AND, OR, NOT, and FANOUT by putting fixed values in one or two of the inputs of the Fredkin gate.
- Show that the Fredkin gate preserves the number of 1s in the system. This is useful, for example, if you want to show how to build a circuit that is implemented by ideal colliding billiard balls.
- A half-adder takes as input two bits x and y , and has two outputs $x \wedge y$ (x AND y) and $x \oplus y$ (x XOR y). Show how to build a half-adder using Fredkin gates (you will need more than two output bits).

5. **Constructing a quantum Toffoli gate**

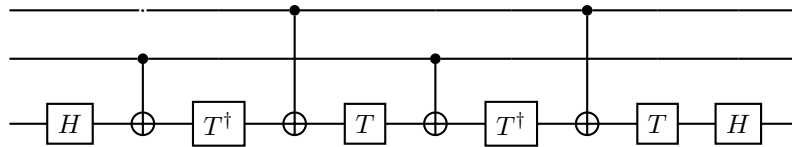- (a) Consider the following quantum circuit, made from one-qubit gates and four CNOT gates:



where the T gate is

$$T = \begin{pmatrix} 1 & 0 \\ 0 & e^{i\pi/4} \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & \frac{1+i}{2} \end{pmatrix}.$$

Show that this nearly yields a Toffoli gate. What unitary transformation does it implement, and how does it differ from a Toffoli gate?

- (b) Explain how you can add one-qubit gates and CNOTs to the first two quantum wires to make this a true Toffoli gate.